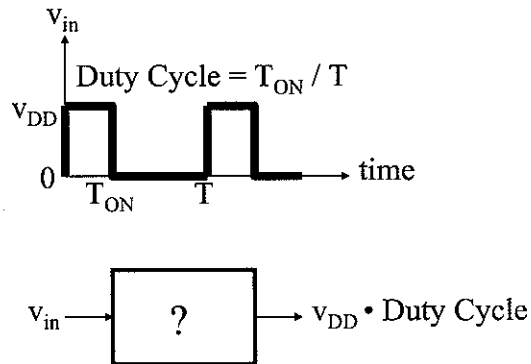


2009 Qualifying Exam
Simon Wong



1. Design a circuit such that with the periodic input waveform shown, the output is approximately a DC voltage of $V_{DD} \cdot \text{Duty Cycle}$.

A low pass filter with bandwidth $\ll 1/T$;

Possible Answers :

R-C low pass filter with $2\pi RC \gg T$

R-L low pass filter with $2\pi L/R \gg T$

L-C filter with $2\pi(LC)^{1/2} \gg T$

(Except for the peaking at resonant frequency, this filter has a low-pass behavior.)

2. If the output has to drive a heavy load (e.g., 1A), how will you modify the circuit ?

Possible Answers :

R-C low pass filter will not be appropriate as the small load resistance will increase the effective bandwidth.

R-L low-pass filter will be fine, but the small load resistance will decrease the effective bandwidth.

L-C filter will not be significantly affected by the load resistance. The peaking will be reduced.

Add a unity gain voltage buffer that is capable of driving the heavy load.