

2015 Quals Questions – Greg Kovacs

Students were given (with important equations) a single-transistor amplifier and asked to derive its gain via simple circuit analysis. If they finished, they were asked a more nuanced question about a slightly modified version of the circuit. The question was undergrad-level only and hints were given if needed.