

2. For the circuit below, sketch the voltage V_x as a function of V_1 , ranging from 0...5V. The MOSFETs obey the ideal square law equation with $\mu C_{ox} W/L = 4\text{mA/V}^2$, and $V_t = 1\text{V}$.

