

# EE Quals 2016

Computer architecture and logic design

Nick McKeown

# Question 1

You are to design the traffic-light controller for the intersection of two streets (A and B). Each street has a single input from a WALK button pushed by pedestrians wishing to cross the street (WALK\_A and WALK\_B). The lights are controlled by two outputs: RED\_A and RED\_B. When RED\_A is 1, then the red light is on and the green light is off for street A. Same for RED\_B.

If no pedestrians present and the WALK buttons are not pushed, the lights alternate between allowing traffic on A and B every 1 minute. If a WALK button is pushed, the current cycle is finished, and then both lights are RED for 1 minute, before returning to the previous alternating A/B cycle.

A: Create a state diagram, and show the state transition table.

B: Encode the states in the minimum number of bits.

C: Design the sequential circuit to implement the state machine.

# Question 2

It's very important for a traffic-light controller to be reliable, and to fail safely. What techniques can we use to reduce the chances of a crash if the system fails?