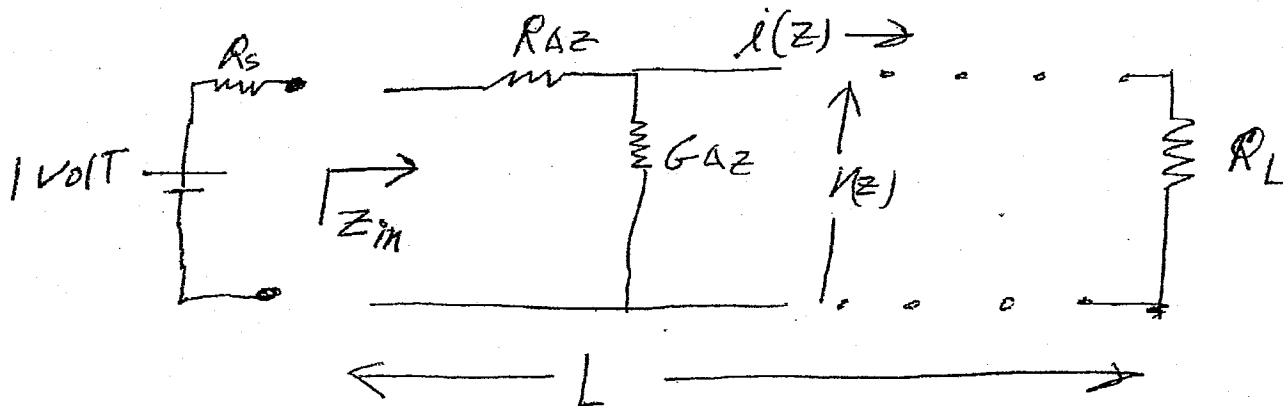


1
Qvals (2007)
Prof. S.E. Harris

Consider a line with distributed resistance R and conductance G connected to a load R_L , with length L



With the source disconnected find the input impedance Z_{in} .

Note that the line is completely described by the differential Equations:

$$\frac{dV}{dz} = -Ri$$

$$\frac{di}{dz} = -GV$$

(1)

where $V(z)$ and $i(z)$ are the voltage and current as a function of position.