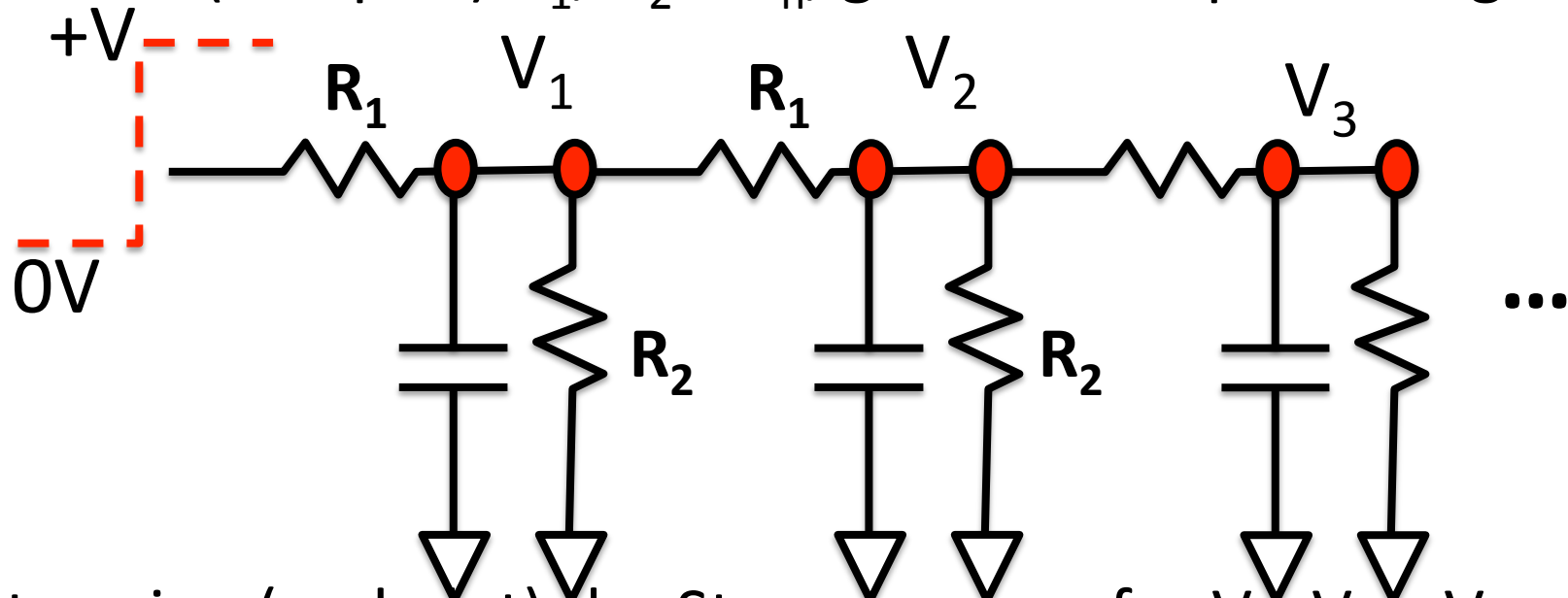


Determine (and plot)  $V_1, V_2 \dots V_n$ , given a dc input voltage  $V_O$



Determine (and plot) the Step response for  $V_1, V_2 \dots V_n$ ,  
As a function of time. Do this for both  $0 \rightarrow +V$  and  $+V \rightarrow 0$