

Name

Start time

1. What are hazards in a logic circuit?
2. Is there a hazard problem for output “a” of the circuit below?
3. If yes, please fix it. If not, why not?
4. Is there any other hazard problem in this circuit? Which ones? What’s the fix? Is it possible to fix those problems without inserting delays?