



Is this device useful for building an amplifier;
 where (and how) would you bias it; what are
 the limitations?