

Name:

Stanford EE Quals 2010
Murmann

1. The circuit below is driven by a voltage ramp that increases linearly with time. Sketch (qualitatively) $V_{\text{out}}(t)$, assuming $V_{\text{out}}(0) = 0\text{V}$.

