

Simon Wong
2016 Quals Questions

Given a common source amplifier with PMOS active load,

1. What is the small signal voltage gain?
2. Show the DC biasing circuits.