

2. For the circuit below, sketch the voltage  $V_x$  as a function of  $V_1$ , ranging from 0...5V. The MOSFETs obey the ideal square law equation with  $\mu C_{ox}W/L = 4\text{mA/V}^2$ , and  $V_t = 1\text{V}$ .

