

Name:

Stanford EE Quals 2007
Murmann

Neglect all capacitances, except the explicitly drawn 1nF capacitor. S1 is an ideal switch; it is closed for $-\infty < t < 0$ and open for $t \geq 0$.

Sketch $V_{out}(t)$, calculate and mark pertinent breakpoints.

