

EE QUALIFYING EXAMINATION

January 23 – 27, 2012

Yoshihisa Yamamoto

1. What is the difference between amplifiers and oscillators?
Discuss the difference in terms of external pumping levels with respect to oscillation threshold and applications.

2. What is the difference between negative conductance oscillators/amplifiers and nonlinear susceptance oscillators/amplifiers?

3. What is the difference between pre-amplifiers and on-line amplifiers?