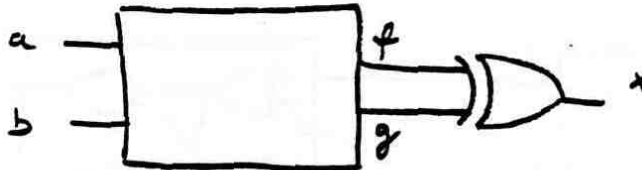


PH.D. QUALIFYING EXAMINATION 1994 / SOLUTIONS

Topic: Logic design and Boolean algebra

NOTE: We are dealing with combinational circuits only.

- 1) An engineer claims correctly that he can replace the XOR gate in the circuit below by a NAND gate.
Can you give an example of a circuit that can fit in the box?




Compare XOR to NAND

| a | b | XOR | NAND |
|---|---|-----|------|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |

XOR differs from NAND on input pattern 00

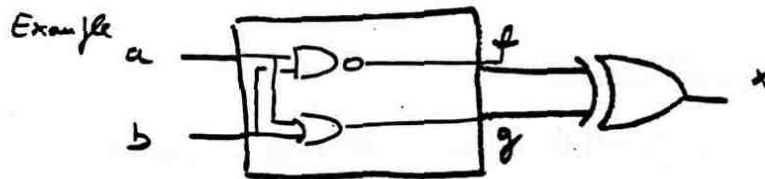The network in the box should not yield 00



- 2) Is the circuit in the box unique?
How can you characterize the class of circuits that fit the box?
Hint: consider functions $f(a,b)$ and $g(a,b)$.

$$f + g = 1$$