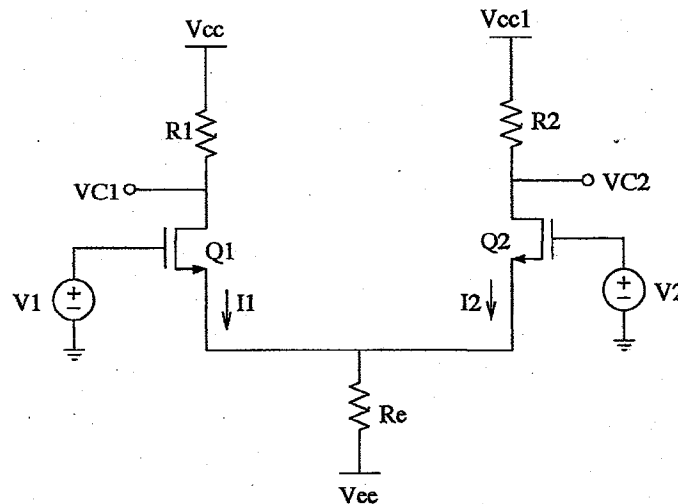


You are stranded on a melting glacier with (1) a hand-full of batteries, (2) a hand-full of resistors, (3) an n-channel MOSFET and (4) a length of wire. You need to somehow build an amplifier to try to send for help.

- ## Problem 2



- The FETs' mode of operation
- The FETs' source voltage