

2012 Quals question:

Students were asked to examine a simple electronic circuit consisting of six commercially available components. The circuit produced rhythmic flashes of light and students were asked to explain the operation of the circuit.

Thanks,  
Greg Kovacs