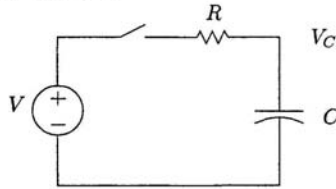


# 2003-2004 Electrical Engineering Qualifying Examination


John Gill

The resistance  $R$ , capacitance  $C$ , and voltage  $V$  in the circuit shown below are independent random variables.



$$\begin{aligned} R &\sim \text{Uniform}[(1 - \delta)R_0, (1 + \delta)R_0] \\ C &\sim \text{Uniform}[(1 - \delta)C_0, (1 + \delta)C_0] \\ V &\sim \text{Uniform}[(1 - \delta)V_0, (1 + \delta)V_0] \\ 0 &< \delta < 1 \\ V_C(t) &= V(1 - e^{-t/RC}) \quad (t > 0) \end{aligned}$$

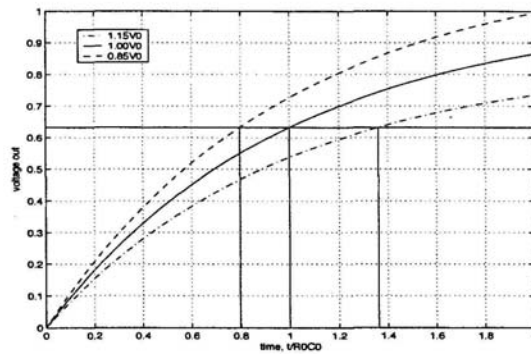The *time constant* of this random RC circuit is defined to be the time  $T$  that is needed for the capacitor to charge to  $V_0(1 - e^{-1})$ . Examples of  $V_C(t)$  and  $T$  are shown in the following figure.



**Question 1** For this random circuit, the time constant is a random variable  $T$ . Find the conditional probability density of  $T$  given fixed values  $R$  and  $C$ .

**Question 2** Find the expected value of the random time constant  $T$ .

**Solution 1** Let  $V_1 = V_0(1 - e^{-1}) = 0.6321 V_0$  denote the nominal threshold voltage, that is, the voltage on the capacitor after one nominal time constant  $R_0 C_0$  when  $V = V_0$ . The time constant random variable  $T$  is a function of  $V$ ,  $R$ , and  $C$ ; it is the solution of the equation

$$V_C(t) = V(1 - e^{-T/RC}) = V_1.$$

Solving the equation is straightforward:

$$\begin{aligned} V(1 - e^{-T/RC}) &= V_1 \Rightarrow 1 - e^{-T/RC} = \frac{V_1}{V} \Rightarrow \\ e^{-T/RC} &= 1 - \frac{V_1}{V} \Rightarrow \frac{T}{RC} = -\ln\left(1 - \frac{V_1}{V}\right) \Rightarrow T = -RC \ln\left(1 - \frac{V_1}{V}\right) \end{aligned}$$