

Mark Horowitz
2016 Quals Questions

My quals question was about a device called a useless box. I had one on my desk that the student could play with, and I asked them how does it work. We then worked through how many states it has, the logical equations for the states, and then how to build it from switches, a battery and a motor.