

Greg Kovacs
2016 Quals Question

Students were shown an analog circuit consisting of two op-amps and some resistors. They were asked to analyze it to explain its function and gain. Hints were provided on the paper. The goal was to demonstrate a clear and organized analytical approach, not necessarily to reach a particular ³answer.²