

Name:

Stanford EE Quals 2008
Murmann

For the circuit below, calculate the low-frequency small-signal gain $A = v_o/v_i$. The MOS device is biased such that it operates in the active region.

