

2015 Quals Questions – Mark Horowitz

Here is a keyboard with 50+ key on it. Assume some mechanical designer created the physical keys giving you 50+ switches. How do you wire up the switches to a chip to generate the information that needs to be sent to a computer to tell what key was pressed?