

Problem 1

Consider an n-channel MOSFET with: μ_n , C_{ox} , W , L , V_t , V_{GS} and V_{DS} .


- What is this transistor's transconductance if operating in triode (linear) mode?
- If this transistor is operating in saturation mode rather than in triode (linear) mode, is the $|\text{gain}|$ of an amplifier larger or smaller? Please show why.

Problem 2

Consider an amplifier with three capacitors C_1 , C_2 & C_3 . Each capacitor "sees" a resistance, found with the other capacitors removed. These resistances are R_1 , R_2 & R_3 .


- You need to increase the high frequency cutoff of the amplifier and can adjust only one capacitor. Which capacitor should you adjust? Why, and how?
- Is this amplifier's dominant pole given by $1/(RC)$, where R is R_1 , R_2 or R_3 and C is C_1 , C_2 or C_3 ?

Problem 3

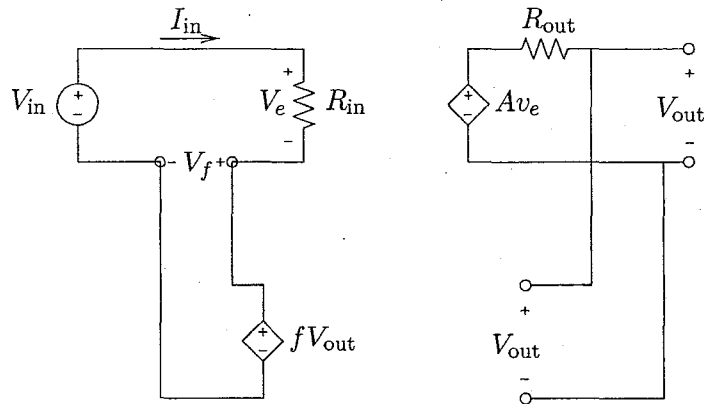

- What is the gain ($G = \frac{V_{out}}{V_{in}}$) of this circuit?
- The input resistance of this circuit is $R_{in,f \neq 0}$. If f is reduced to zero ($f = 0$), the input resistance is $R_{in,f=0}$. How is $R_{in,f \neq 0}$ related to $R_{in,f=0}$?

Problem 4

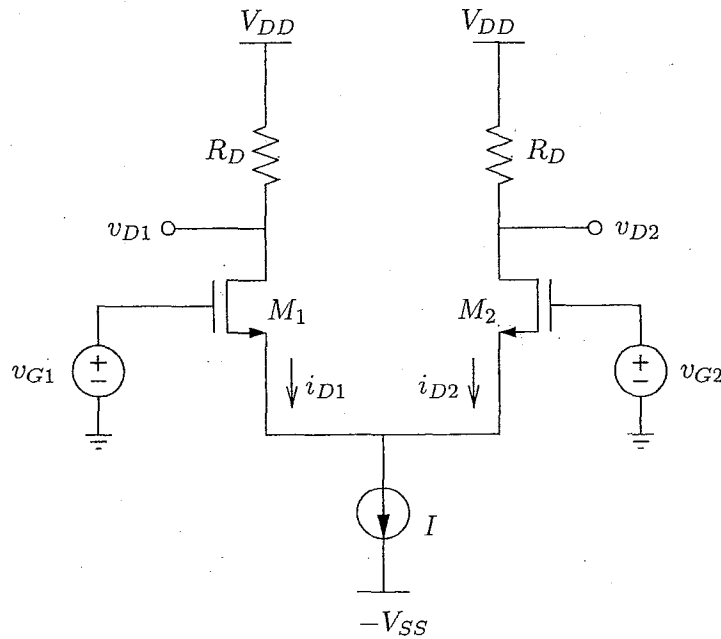

- This is a symmetrical differential amplifier, with M_1 and M_2 operating in saturation mode.
 - When there is no differential input voltage ($v_{ID} = v_{GS1} - v_{GS2} = 0$) the tail current divides evenly between the two arms ($i_{D1} = i_{D2} = I/2$).
 - The gate to source voltages must then also be equal: $V_{GS0} = v_{GS1} = v_{GS2}$.
 - And $\frac{I}{2} = K_N(V_{GS0} - V_t)^2$ where $K_N = \frac{1}{2}\mu_n C_{ox} \frac{W}{L}$.
- (a) What is the minimum differential input voltage (v_{ID}) that can be applied to cause all current to flow through M_1 ? Please write expression in terms of $V_{GS0} - V_t$.
- (b) What is the common mode rejection ratio? What is it for this circuit (assume differential input and differential output)?

Problem 5


Please describe the major sub-circuits of an op-amp, and the critical design considerations of each.

Problem 1

You are stranded on a melting glacier with (1) a hand-full of batteries, (2) a hand-full of resistors, (3) an n-channel MOSFET and (4) a length of wire. You need to somehow build an amplifier to try to send for help.

- With just these parts, can you build an amplifier? Please "chisel circuit in the ice" & explain its operation.
- What is your goal with the battery(batteries)?
- What is your goal with the resistor(s)?
- You now find another MOSFET in your coat pocket, and its a p-FET. Should you modify your circuit? Why?
- You suspect that your amplifier's high-frequency cutoff is too low to be useful. What should you look for (and change if you could) in the circuit and MOSFETs?


Problem 2

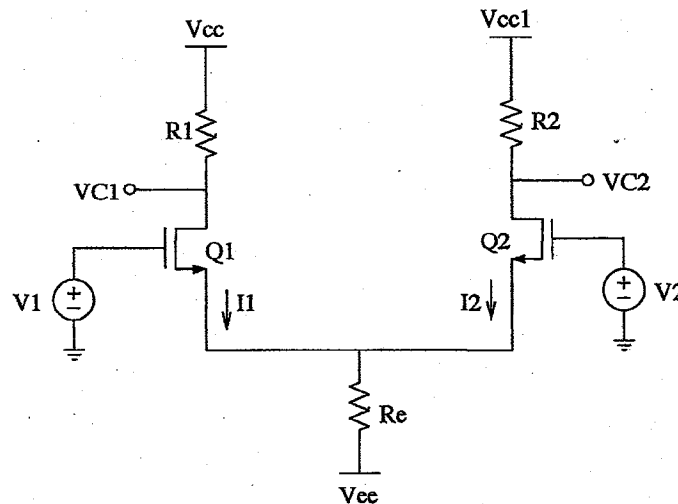

Consider this symmetric differential amplifier. Please explain how the following change when a common-mode voltage is ramped up ($V_{ee} \rightarrow V_{cc}$) at the inputs:

- The FETs' mode of operation
- The FETs' source voltage

Problem 3

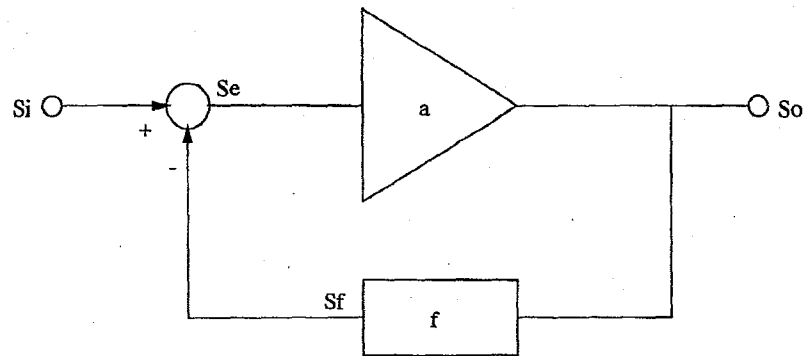

Consider this idealized feedback configuration.

- (a) Please derive an expression for the closed-loop gain (A).
- (b) Please derive an expression for the closed-loop 3dB frequency ($\omega_{3dB,CL}$) when the basic amplifier (a) is now modeled as a one pole system:

$$a(s) = \frac{a_o}{1 + \frac{s}{\omega_{3dB}}}$$

where a_o is the open-loop DC gain and ω_{3dB} is the 3dB open-loop frequency.

- (c) Does the addition of feedback increase the gain-bandwidth product? Why or why not?

Problem 4

Please describe the major sub-circuits of an op-amp, and the critical design considerations of each.

1. Does the transconductance of a MOSFET depend linearly on I_{DS} ? Why (please derive)?
2. To carry the same amount of current under the same bias conditions, should a PMOS transistor be made wider, narrower, or the same as a nearby NMOS? Why (in physical terms)?
3. Please sketch an NMOS differential amplifier with tail current of 1 mA (i.e., a current source of 1 mA between source node and ground). What happens to V_{SOURCE} when the common-mode input voltage is increased? Why?
4. Before the days of digital computers, or even calculators, if you wanted to electronically calculate the natural logarithm (\ln) of a number how could you do it? Please sketch and/or write equations to explain.
5. If you wanted to amplify the signal from a photodiode (which acts like a weak current source) with a common source amplifier, should you connect a resistor so as to form a series-x or a shunt-x feedback amplifier? Or is feedback not needed? Please explain.
6. Please describe the major sub-circuits of an op-amp, and the critical design considerations of each.