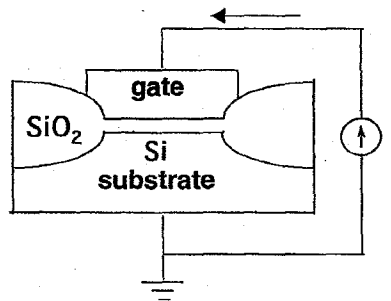


PhD Quals Question 2006-07
Krishna Saraswat



If the device shown in the figure is connected to a current source what kind of current voltage characteristics would result?